

# Power converters AC/DC and DC/AC - MM3

## Single phase Thyristor converters

### Content MM3


1. Summary from MM2
2. Thyristor circuits and their control
3. Single phase converter ( $L_s = 0$ )
4. Single phase converter ( $L_s \neq 0$ )
5. Practical circuits
6. Inverter mode
7. Exercises

## 2. Thyristor circuits and their control

- Diode rectifier
  - non-controllable DC-link-voltage
  - Large inrush currents


- Thyristor converter
  - Controllable DC-link-voltage
  - Controllable inrush currents

### Principle rectifier/inverter

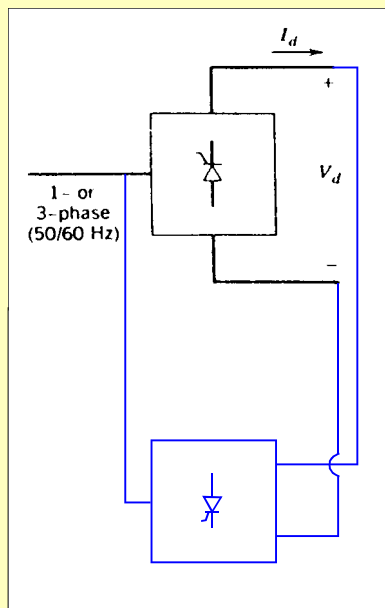


Battery chargers  
DC-motor control ( $E = k\omega$ )

### Operation area

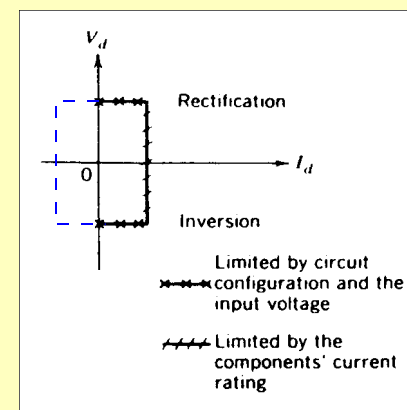

## 2. Thyristor circuits and their control



### Thyristor

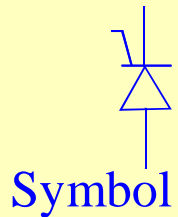

Model


- Turned on with a gate trigger signal
- Closed only with a reversed biased voltage  $\rightarrow$  Line commutated
- 6 kV, 6kA (single Thyristor)
- Later more details about Thyristors

### Principles

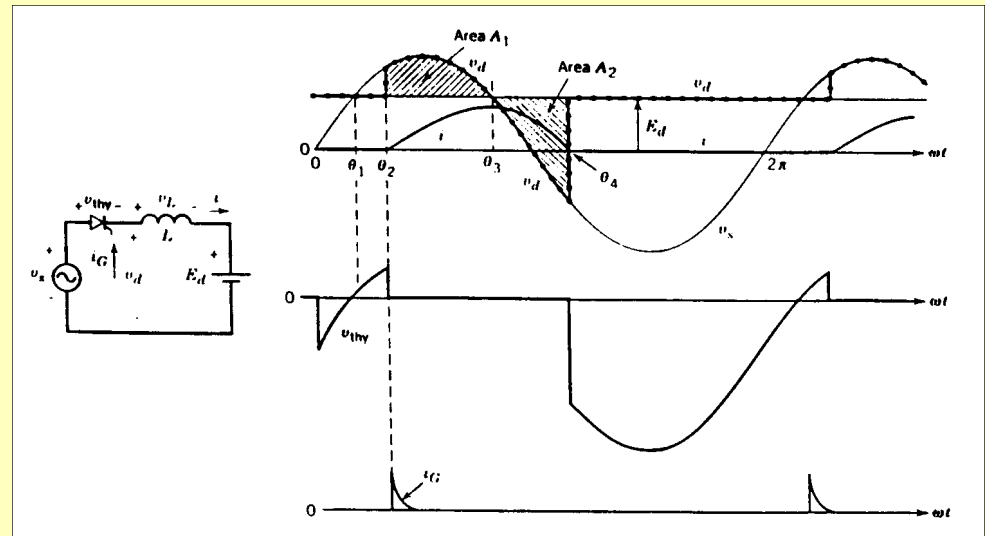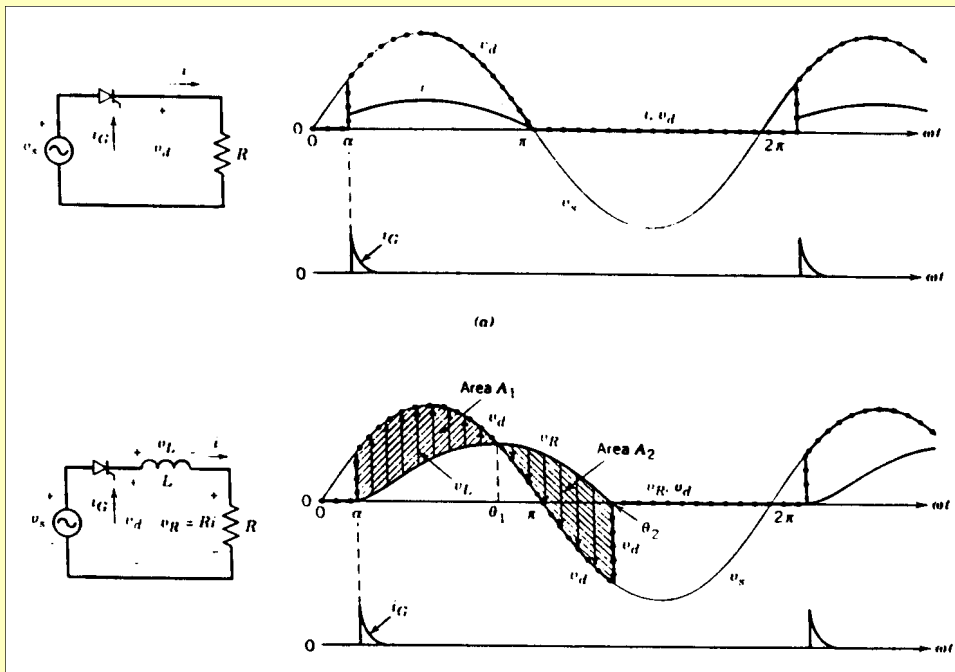


## 2. Thyristor circuits and their control

### Gate trigger control circuit

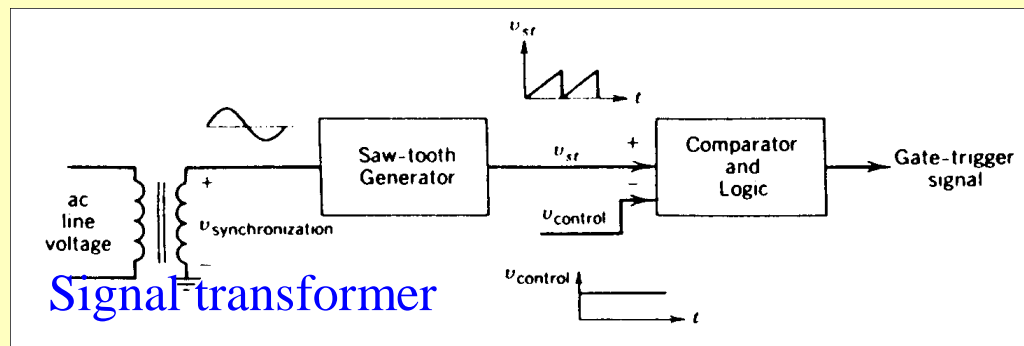

### Delay angle $\alpha$

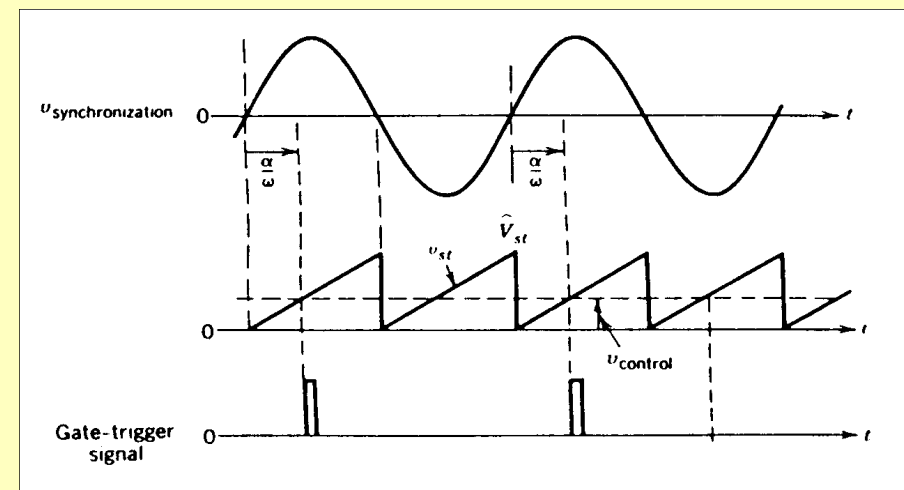


### Delay angle $\alpha$


$$\alpha^\circ = 180^\circ \frac{v_{\text{control}}}{\hat{V}_{st}}$$

### 3. Single phase converter ( $L_s = 0$ )

**Circuit (ideal)**

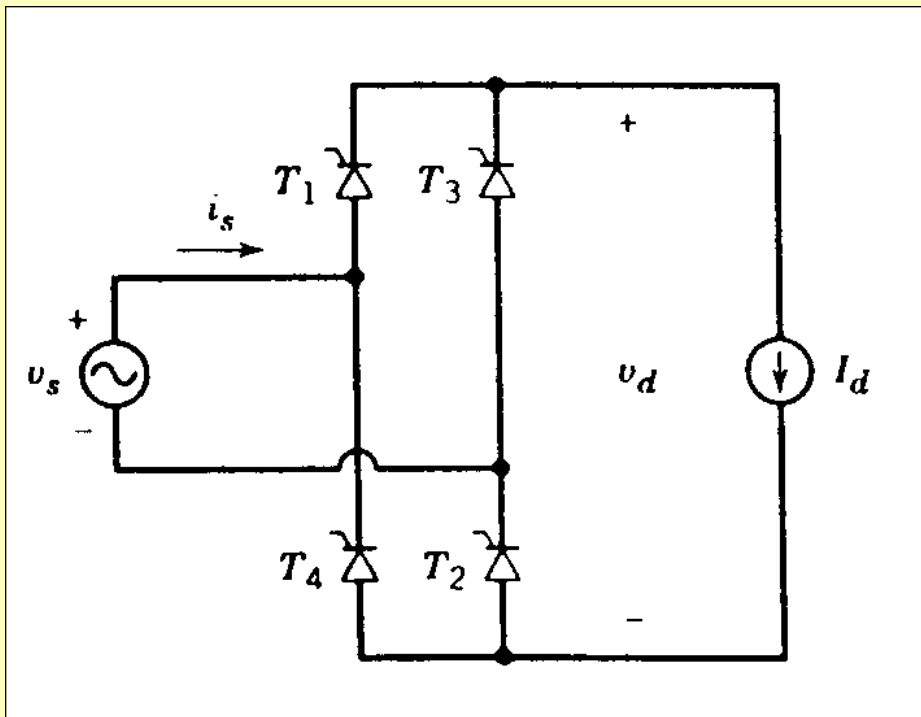


**Reorganized**

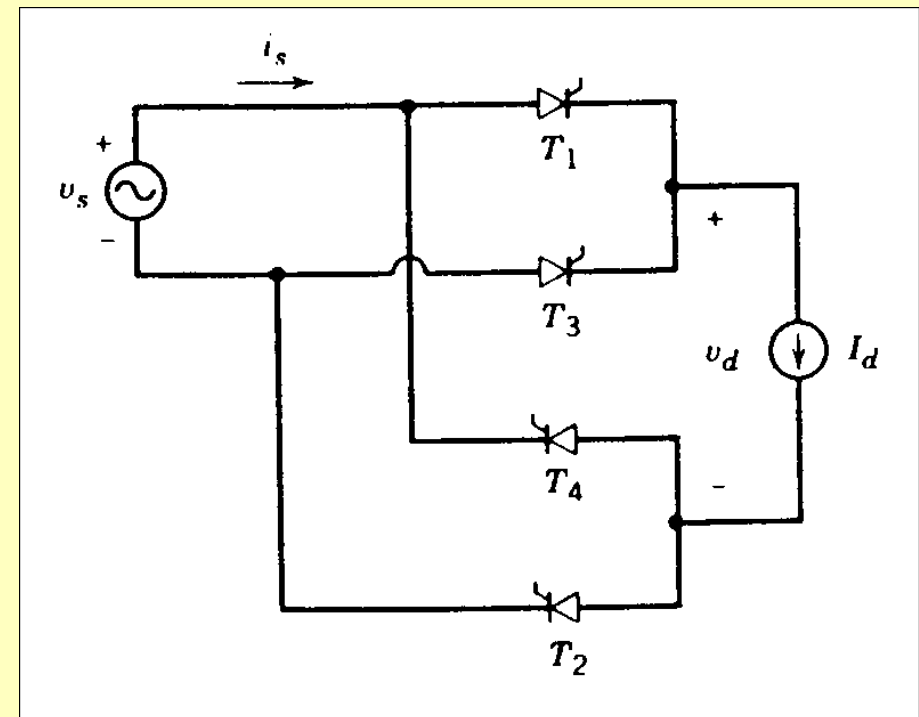

## Waveforms
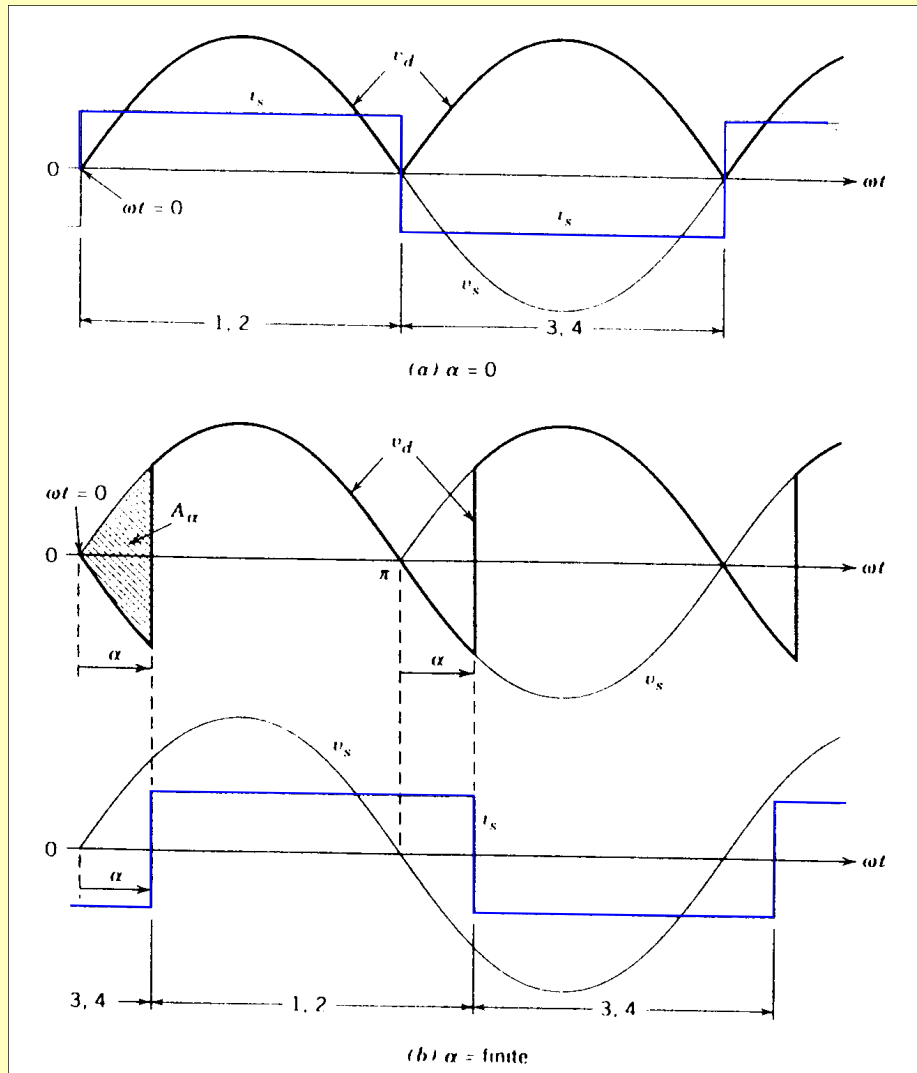
### 3. Single phase converter ( $L_s = 0$ )



## Average voltage


$$V_{d\alpha} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2}V_s \sin \omega t d(\omega t) = \frac{2\sqrt{2}}{\pi} V_s \cos \alpha = 0.9V_s \cos \alpha$$

## Power


$$P = I_d \left( \frac{1}{T} \int_0^T v_d dt \right) = I_d V_d = 0.9V_s I_d \cos \alpha$$

### 3. Single phase converter ( $L_s = 0$ )


#### Average voltage vs. delay angle

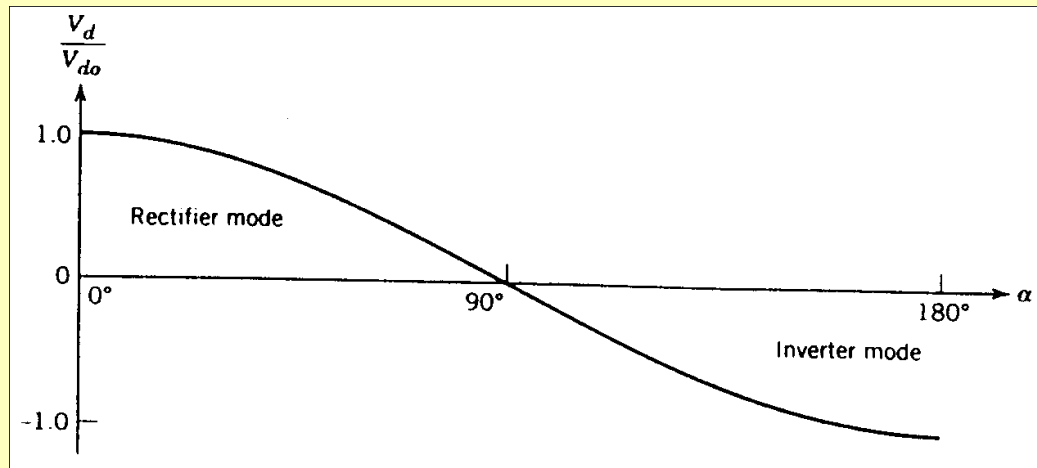


#### Harmonics

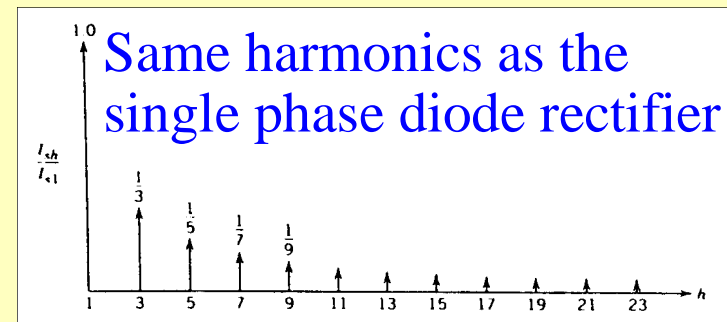

#### Current

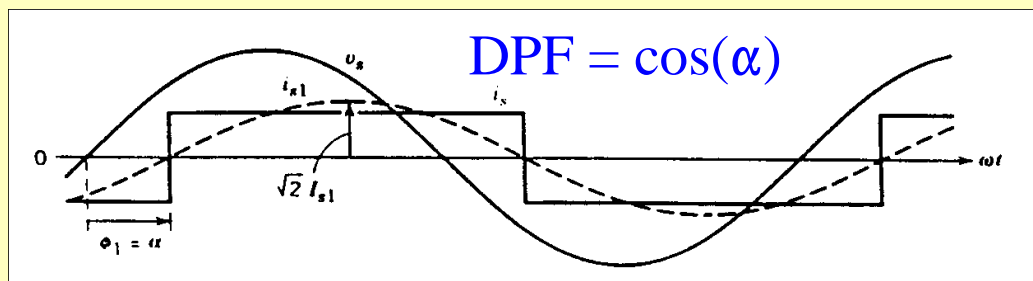

#### P, S, Q

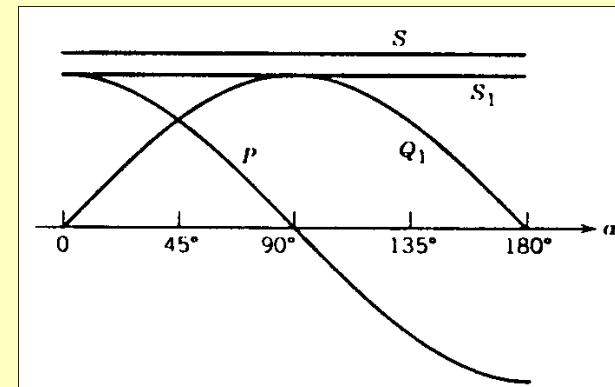


$$P_1 = V_s I_{s1} \cos(\phi_1)$$

$$Q_1 = V_s I_{s1} \sin(\phi_1)$$


$$S_1 = \sqrt{P_1^2 + Q_1^2}$$

## 4. Single phase converter ( $L_s \neq 0$ )

### Circuit

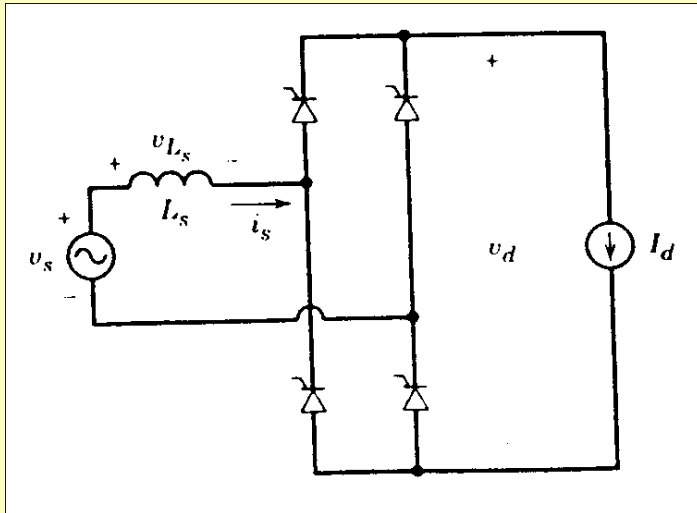

### Waveforms

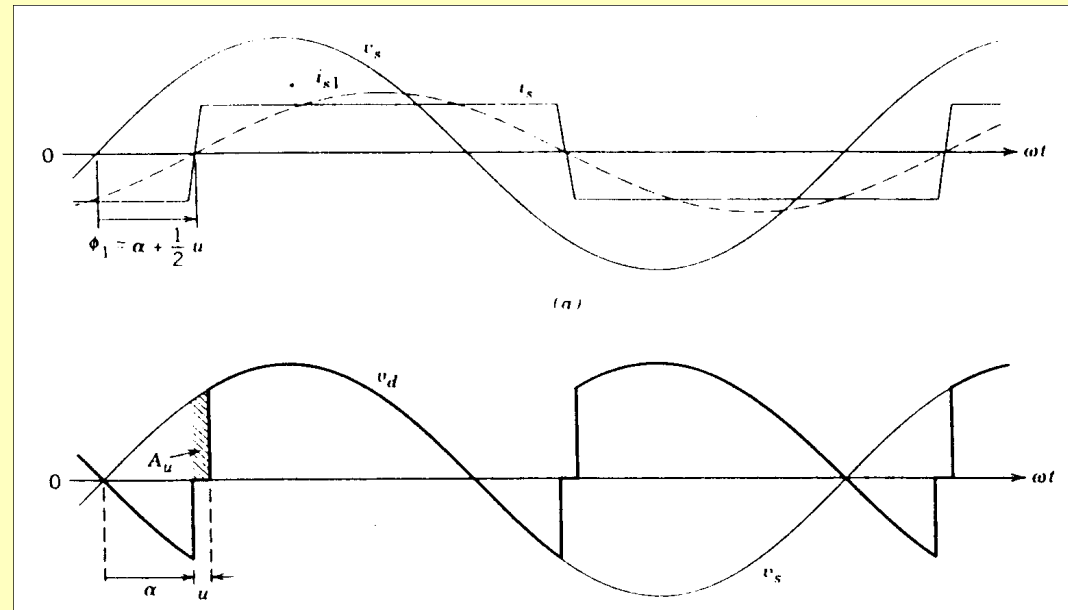

### Voltage time integral

$$A_u = \sqrt{2}V_s[\cos \alpha - \cos(\alpha + u)] = 2\omega L_s I_d$$

### Commutation interval


$$\cos(\alpha + u) = \cos \alpha - \frac{2\omega L_s I_d}{\sqrt{2}V_s}$$

### Average voltage


$$V_d = 0.9V_s \cos \alpha - \frac{2}{\pi} \omega L_s I_d$$

## 5. Practical circuits

### DC-motor

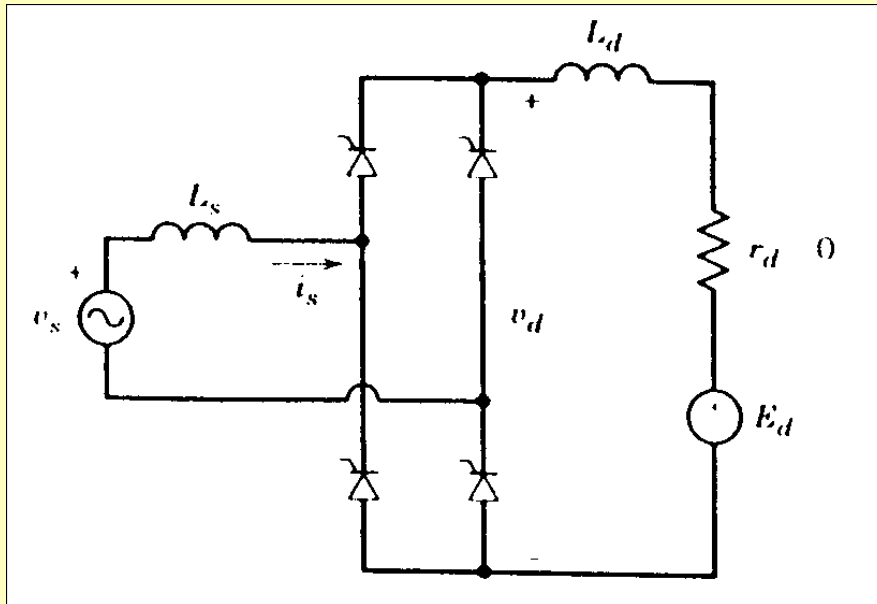


### Waveforms

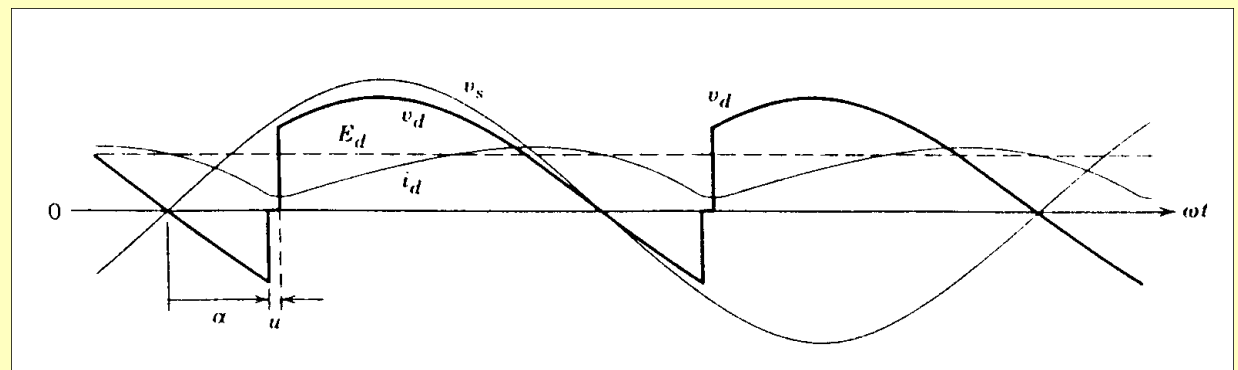


## 5. Practical circuits

### Discontinuous operation

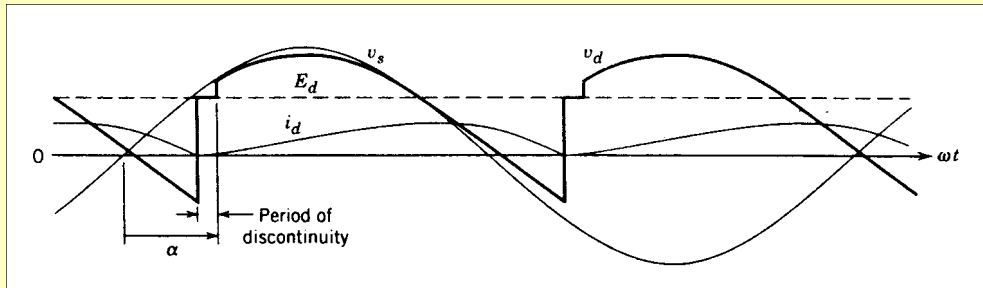


### $V_d$ versus $I_d$

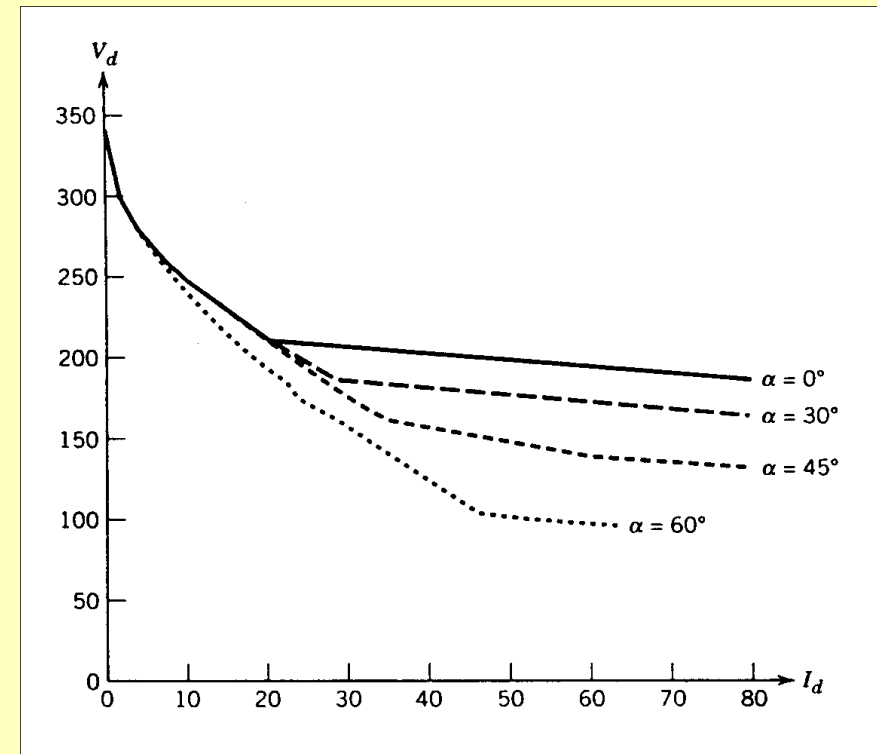


## 6. Inverter mode

### Circuit (constant current)

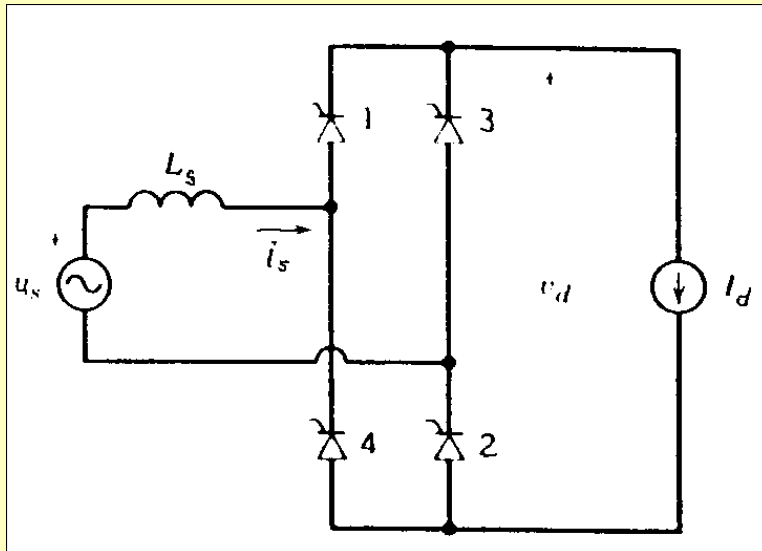


### Waveforms ( $\alpha > 90^\circ$ )

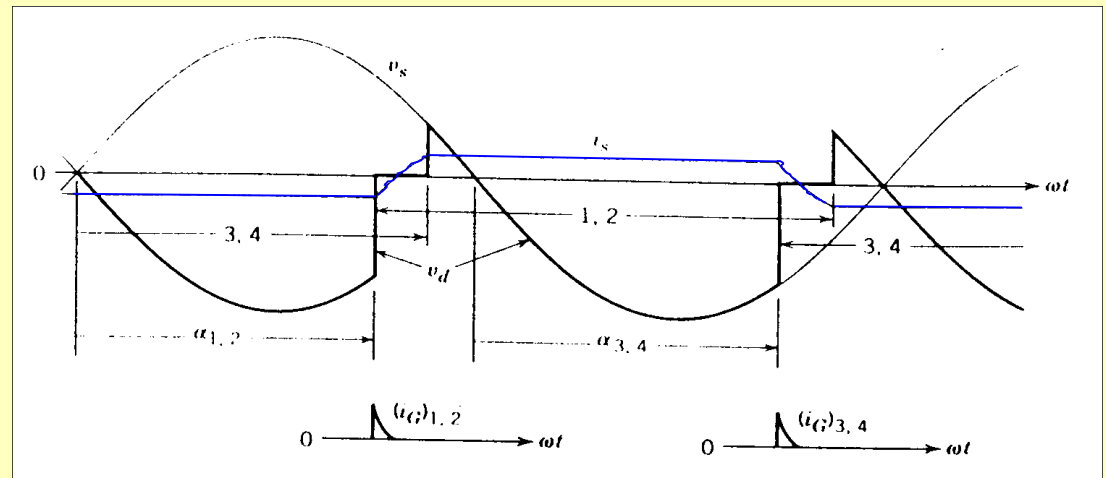


## 6. Inverter mode


### Circuit (Constant voltage)

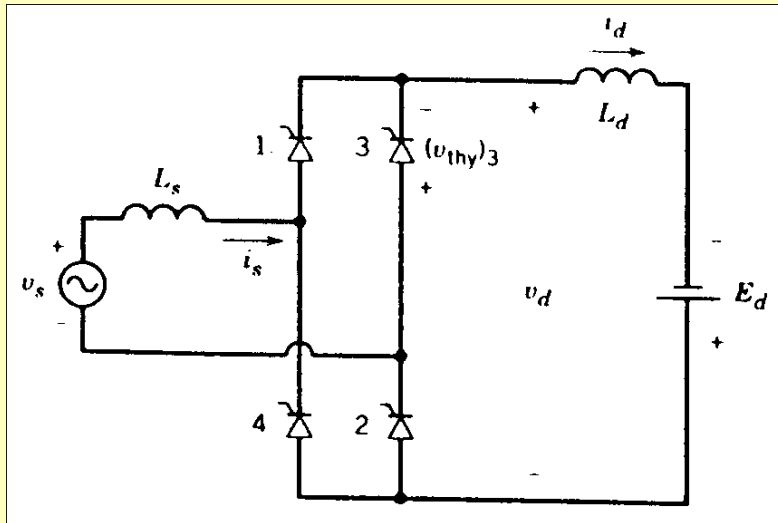

### Characteristics

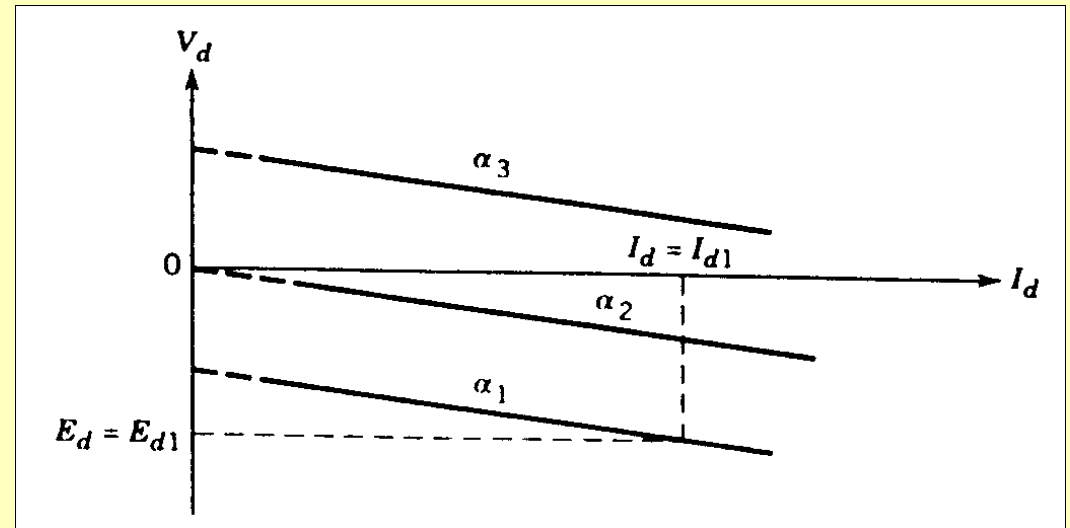

### Waveform

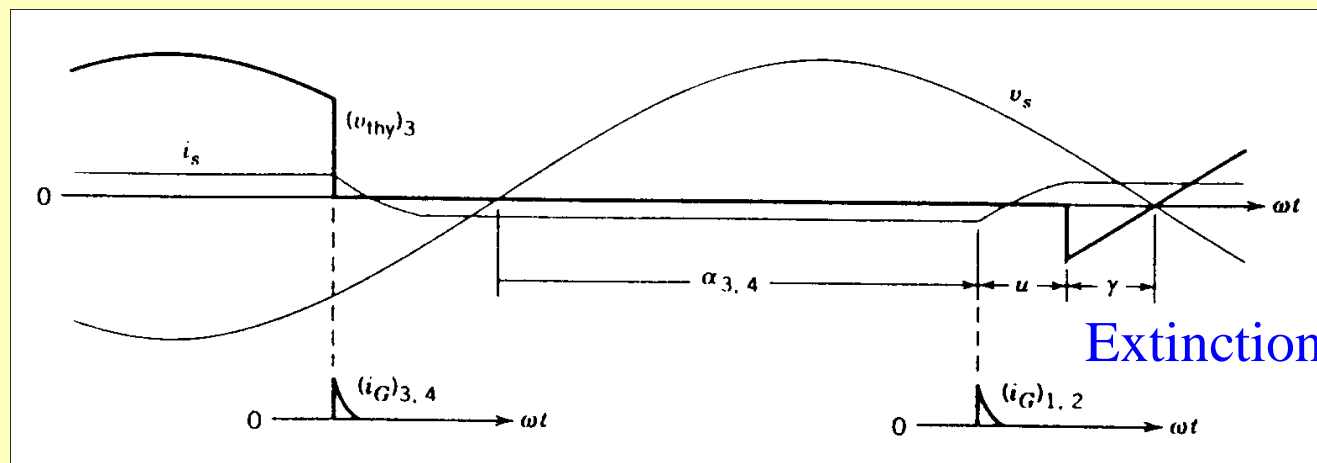

Extinction angle

## 7. Exercises

### **Exercise 6.3 + Exercise 6.5 in Mohan**