


## Using Digital Potentiometers to Design Low-Pass Adjustable Filters

Author: Bonnie C. Baker  
Microchip Technology Inc.

### INTRODUCTION

The most common filter found in a data acquisition system signal path is a low-pass filter. This type of filter is usually used to reduce A/D Converter (ADC) aliasing errors. If there is more than one signal that is applied to the A/D converter through a multiplexer, each signal source may have its own set of filter requirements (i.e., settling time, fast transition region, etc.). Consequently, a variety of filters may be required in the circuit prior to the multiplexer. Usually these filters are implemented with operational amplifiers (op amps) in combination with fixed resistors and capacitors.

An alternative filter design solution is to have one filter following the multiplexer. In this circuit, the low-pass filter would need to be programmable. The obvious advantage of having the filter serve many analog inputs is that there is a reduction in chip count. An example of this type of approach is shown in Figure 1.

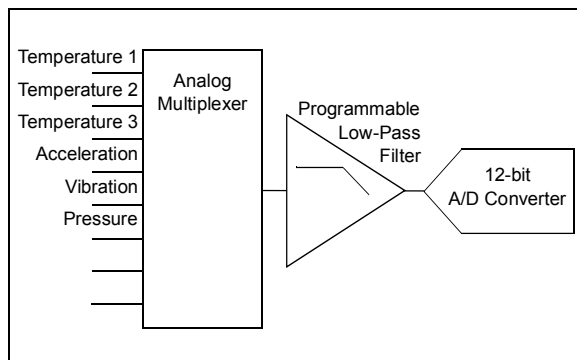


**FIGURE 1:** If a programmable low-pass filter is used in the application circuit, it can be placed after the analog multiplexer. The programmability of the filter allows for a wide variety of input signals.

### Programmable Low-Pass Filters

In this application note, a programmable, second-order, low-pass filter will be presented in four different scenarios. The first three scenarios will illustrate how a dual digital potentiometer and a single amplifier can be configured for low-pass second-order Butterworth, Bessel and Chebyshev responses with a programma-


ble corner frequency range of 1:100. An example of the digital potentiometer setting for these designs is summarized in Tables 1, 2 and 3. The fourth scenario will show the same circuit design, where all three approximation methods (Butterworth, Bessel and Chebyshev) can coexist with a programmable corner frequency range of 1:10. An example of the digital potentiometer settings for this combination of approximation methods is summarized in Table 4.

Figure 2 shows the details of a single-supply, unity gain, second-order, programmable low-pass Sallen Key filter. This filter is implemented with two resistors and two capacitors. The two resistors in this circuit are replaced with the dual MCP42100, 100 k $\Omega$ , 8-bit, digital potentiometer.

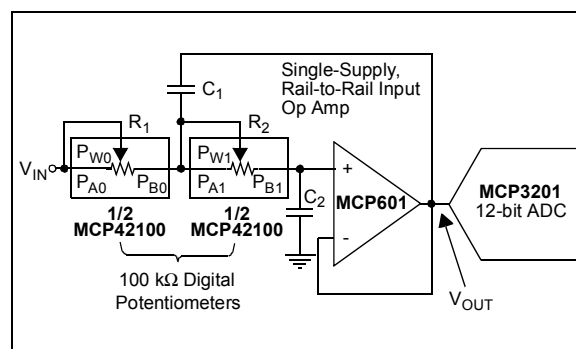


**FIGURE 2:** The combination of a dual digital potentiometer and a single-supply, rail-to-rail amplifier can be used to construct a programmable, second-order, Sallen-Key, low-pass filter.

Digital potentiometers can be used to adjust system reference levels, gain errors and offset errors, while offering the added capability of digital adjustment control. Devices such as Microchip's MCP41XXX and MCP42XXX digital potentiometer families have three resistive terminals for the single versions (MCP41010, MCP41050 and MCP41100) and six resistive terminals for the dual versions (MCP42010, MCP42050 and MCP42100) and are illustrated in Figure 3. The MCP41010 and MCP42010 are both 10 k $\Omega$  potentiometers. The MCP41050 and MCP42050 are both 50 k $\Omega$  potentiometers, while the MCP41100 and 42100 are both 100 k $\Omega$  potentiometers.

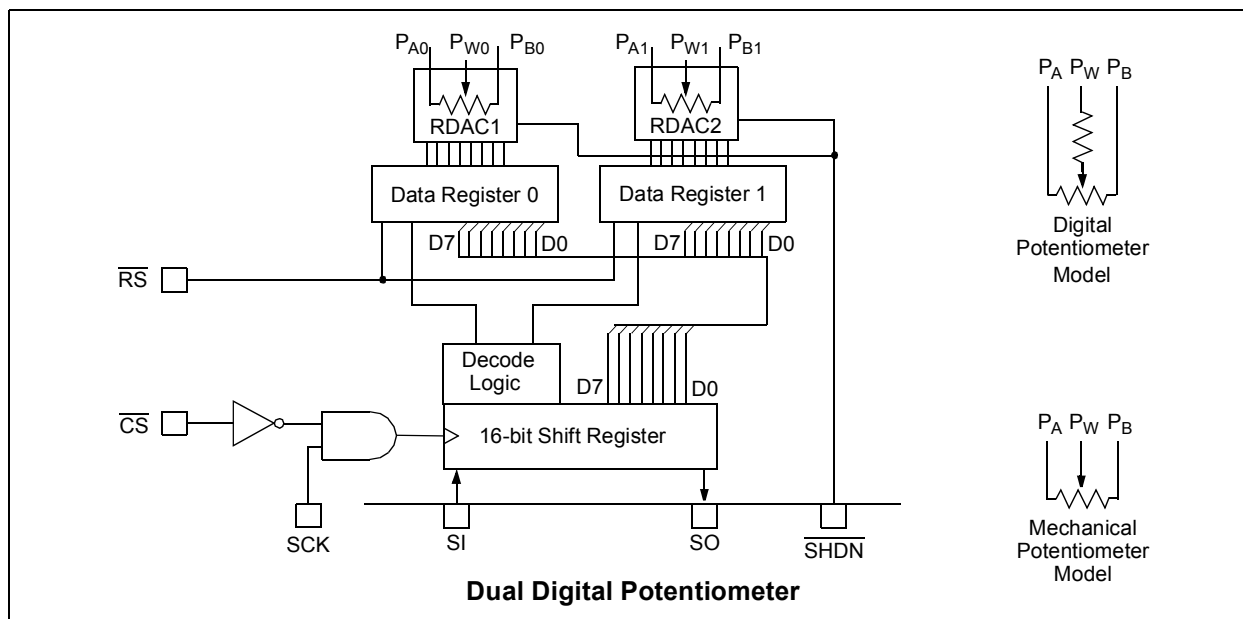

**FIGURE 3:** The operation of the digital potentiometer as compared to the mechanical potentiometer is functionally the same. The adjustment of the digital potentiometer is done with a serial code to the device. Although the mechanical potentiometer provides simplicity, the digital potentiometer provides flexibility and reliability.

The potentiometer can be configured for two modes: the Rheostat mode and Voltage Divider mode. In the Rheostat mode, the wiper (terminal  $P_W$ ) is shorted to either the  $P_A$  or  $P_B$  terminal of the device. This configuration is shown in Figure 4. When used in the Voltage Divider mode (Figure 4.b), all three terminals are connected to differing nodes in the circuit. For the analog filter example in this application note, the digital potentiometer will be configured in the Rheostat mode.

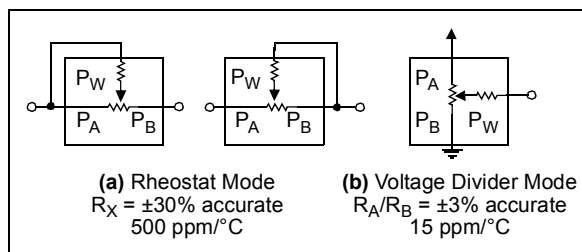

**FIGURE 4:** A digital potentiometer can be configured in the (a) Rheostat mode or (b) Voltage Divider mode.

The operational amplifier used in this application circuit is a single-supply, rail-to-rail out device. The MCP601 is a single amplifier that belongs to the MCP601/2/3/4 family of operational amplifiers. The MCP603 is also a single amplifier with a Chip Select feature. The dual version is the MCP602, while the quad version is the MCP604. These amplifiers are optimized for high speed, low offset voltage and single-supply operation.

By adjusting the two digital potentiometers in Figure 2, the frequency cutoff and the filter approximation method of this second-order low-pass filter can be changed.

The design equation for this low-pass filter configuration is:

$$\frac{V_{OUT}}{V_{IN}} = \frac{K/(R_1 R_2 C_1 C_2)}{s^2 + s(1/R_1 C_1 + 1/R_2 C_1 + 1/R_2 C_2 - K/R_2 C_2) + 1/R_1 R_2 C_1 C_2}$$

Where:  $K = 1$

With this formula, the appropriate resistance and capacitance can be calculated. An alternative to this tedious design exercise is to determine the capacitor and resistor values using the FilterLab® software, a filter design program that can be downloaded from Microchip's web site at [www.microchip.com](http://www.microchip.com).

The Circuit screen in this program allows the user to adjust the capacitors to desired values ( $C_1$  and  $C_2$  per Figure 2). When these capacitors are set, the software changes the resistors in the circuit to appropriate values for the circuit implementation. There may be a corner frequency and stability error with low-pass filters that are designed at frequencies higher than 100 kHz. This error is introduced by the parasitic capacitance of the digital potentiometer. As a general guideline,  $C_1$  and  $C_2$  should be larger than 10 nF.

For more detailed information concerning anti-aliasing filters, please refer to Microchip's Application Note 699, entitled "Anti-Aliasing, Analog Filters for Data Acquisition Systems" (DS00699).

**TABLE 1: A BUTTERWORTH FILTER DESIGN ADJUSTING THE RESISTORS THROUGH A DIGITAL POTENTIOMETER**

Specifications: Programmable cutoff frequency range of 100 Hz to 10 kHz by using capacitors of $C_1 = 0.047 \mu\text{F}$ , $C_2 = 0.018 \mu\text{F}$ and adjusting the resistors through a digital potentiometer.						
Cutoff Frequency, Hz	FilterLab Calculated 1% $R_1$ Value, $k\Omega$	Closest Nominal Digital Pot. $R_1$ Value, $k\Omega$	Digital Pot. $R_1$ Code, decimal	FilterLab Calculated 1% $R_2$ Value, $k\Omega$	Closest Digital Pot. $R_2$ Value, $k\Omega$	Digital Pot. $R_2$ Code, decimal
100	32.2	32.031	82	92.8	92.969	238
200	16.1	16.016	41	46.4	46.484	119
300	10.7	10.156	26	30.9	30.859	79
1000	3.22	3.125	8	9.28	9.375	24
2000	1.61	1.563	4	4.64	4.688	12
3000	1.07	1.172	3	3.09	3.125	8
10000	322	0.391	1	928	0.781	2

### Butterworth Second-Order Low-Pass Filters

When a Butterworth filter is required, the Sallen Key configuration shown in Figure 2 can have an adjustable frequency range of 1:100. The frequency behavior of the Butterworth filter is maximally flat in the magnitude response in pass band. The rate of attenuation in transition band is better than the Bessel filter, though not as good as the Chebyshev filter. There is no ringing in the stop band. The step response of the Butterworth filter has some overshoot and ringing in the time domain, though this is less than the Chebyshev filter.


The capacitor values in this circuit are kept constant while the resistive elements are adjusted. The two capacitors should be carefully selected to be constants in the FilterLab software so that the digital potentiometer resistances are the only values that are changing. These capacitive values can easily be found in the FilterLab software through experimentation.

As an example, a programmable second-order, low-pass Butterworth filter with a corner frequency that ranges from 100 Hz to 10 kHz can be designed by setting  $C_1 = 0.047 \mu\text{F}$  and  $C_2 = 0.018 \mu\text{F}$ . The values calculated by the FilterLab software for this filter design are summarized in Table 1. Table 1 also includes the closest values for  $R_1$  and  $R_2$  from the digital potentiometer, along with the digital program code for the MCP42100.


Verification of the performance of the Butterworth filters that use 1% discrete resistors can be performed with the SPICE listing that is provided as an output from the FilterLab software. The SPICE simulations for the 100 Hz, 200 Hz, 300 Hz and 1,000 Hz filters using the values calculated by the FilterLab software are shown in Figure 5.

To validate the digital potentiometer design, SPICE simulations can be performed on the Butterworth filters using the digital potentiometer values. The 100 Hz, 200 Hz, 300 Hz and 1,000 Hz filters using the calculated nominal resistance values of the digital potentiometers, per Table 2, are shown in Figure 6.

From these two SPICE simulations, it is easy to see that the filters from Figure 5 behave fundamentally the same over frequency as compared to Figure 6.

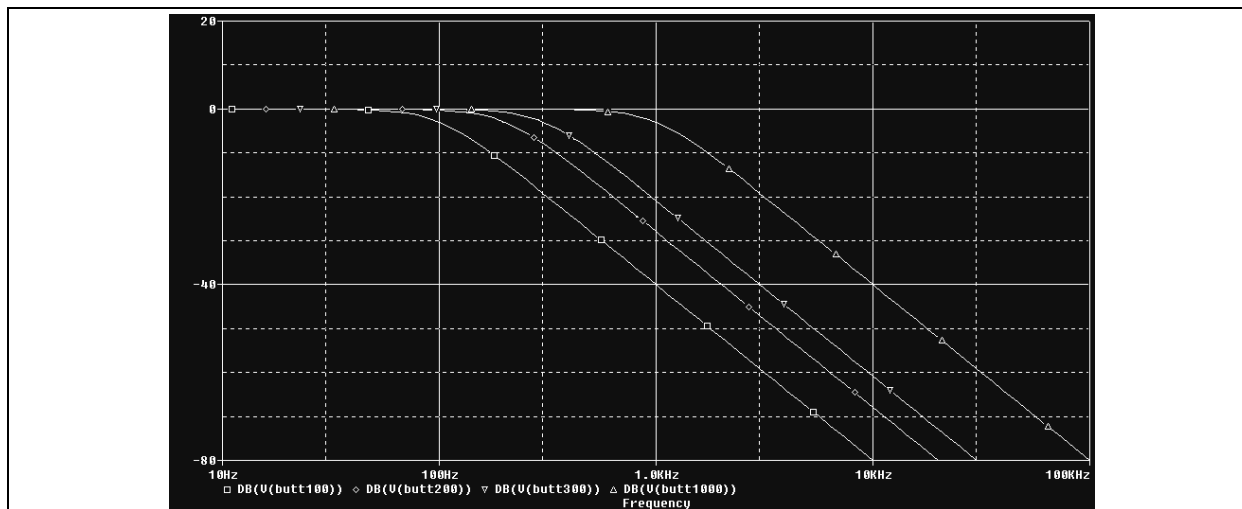

**FIGURE 5:** SPICE simulation of four Butterworth, second-order low-pass filters with corner frequencies of 100 Hz, 200 Hz, 300 Hz and 1,000 Hz. In this simulation, 1% resistor values were used.

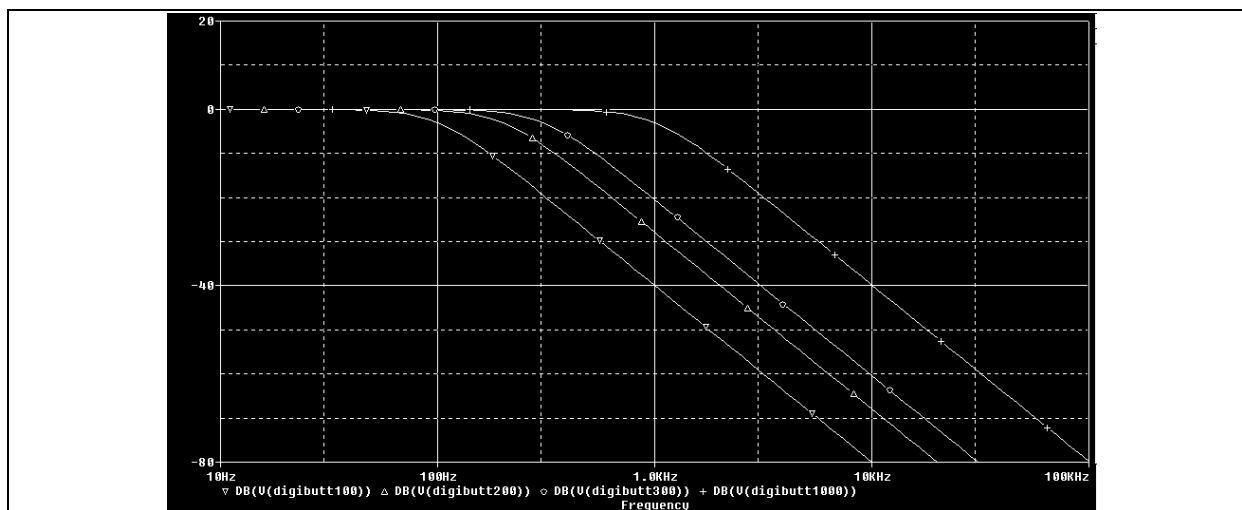

**FIGURE 6:** SPICE simulation of four Butterworth, second-order low-pass filters with corner frequencies of 100 Hz, 200 Hz, 300 Hz and 1,000 Hz. In this simulation, nominal digital potentiometer resistor values, per Table 1, were used.

**TABLE 2: A PROGRAMMABLE BESSEL FILTER DESIGN USING A DUAL 100 K $\Omega$  DIGITAL POTENTIOMETER.**

Specifications: A programmable Bessel filter with a cutoff frequency range of 100 Hz to 10 kHz can be implemented with  $C_1 = 0.033 \mu\text{F}$ ,  $C_2 = 0.018 \mu\text{F}$  and a dual 100 k $\Omega$  digital potentiometer.

Cutoff Frequency, Hz	FilterLab Calculated 1% $R_1$ Value, k $\Omega$	Closest Nominal Digital Pot. $R_1$ Value, k $\Omega$	Digital Pot. $R_1$ Code, decimal	FilterLab Calculated 1% $R_2$ Value, k $\Omega$	Closest Digital Pot. $R_2$ Value, k $\Omega$	Digital Pot. $R_2$ Code, decimal
100	28.7	28.516	73	91.5	91.406	234
200	14.3	14.453	37	45.7	43.75	117
300	9.57	9.375	24	30.5	30.469	78
1000	2.87	2.734	7	9.15	8.984	23
2000	1.43	1.563	4	4.57	4.688	12
3000	0.957	0.781	2	3.05	3.125	8
10000	0.287	0.391	1	0.915	0.781	2

## Bessel Second-Order Low-Pass Filters

When a Bessel filter is desired, the Sallen Key configuration, shown in Figure 2, can have an adjustable frequency range of 1:100. As with the Butterworth filter, the frequency response of the Bessel filter has a flat magnitude response in the pass band. Following the pass band, the rate of attenuation in the transition band is slower than the Butterworth or Chebyshev. Finally, there is no ringing in the stop band. This filter has the best step response of all of the filters mentioned in this application note, with very little overshoot or ringing.

In Table 3, a programmable Bessel filter is designed with a corner frequency range of 100 Hz to 10 kHz, by setting  $C_1 = 0.033 \mu\text{F}$  and  $C_2 = 0.018 \mu\text{F}$ . Once again, in the FilterLab software, the capacitor values are kept constant, while the resistive elements are adjusted.

## Chebyshev 2<sup>nd</sup> Order Low-Pass Filters

The filter in Figure 2 can also be designed in the Chebyshev approximation for an adjustable range of 1:100. With the Chebyshev filter, the frequency behavior exhibits a ripple in the pass-band that is determined by the specific placement of the poles in the circuit design. With the design discussed in this application note, the ripple is 3 dB. In general, an increase in ripple magnitude will lessen the width of the transition band. The rate of attenuation in the transition band is steeper than Butterworth and Bessel filters. Although there is ringing in the pass-band region with this filter, the stop band is devoid of ringing. The step response has a fair degree of overshoot and ringing.

An example of the digital potentiometer settings for a 2nd order, low-pass Chebyshev filter is given in Table 3.

**TABLE 3: CHEBYSHEV FILTER DESIGN**

Specification: Chebyshev, 3 dB Ripple, 100 to 10 kHz cutoff, $C_1 = 0.15 \mu\text{F}$ , $C_2 = 0.015 \mu\text{F}$						
Cutoff Frequency, Hz	FilterLab Calculated 1% $R_1$ Value, $k\Omega$	Closest Nominal Digital Pot. $R_1$ Value, $k\Omega$	Digital Pot. $R_1$ Code, decimal	FilterLab Calculated 1% $R_2$ Value, $k\Omega$	Closest Digital Pot. $R_2$ Value, $k\Omega$	Digital Pot. $R_2$ Code, decimal
100	21.0	21.094	54	75.6	75.781	194
200	10.5	10.547	27	37.8	37.891	97
300	7.01	7.031	18	25.2	25.391	65
1000	2.10	1.953	5	7.56	16.016	41
2000	1.05	1.563	4	3.78	3.9063	10
3000	0.701	0.781	2	2.52	2.344	6
10000	0.210	0.391	1	0.756	0.781	2

**TABLE 4: THE BUTTERWORTH, BESSEL AND CHEBYSHEV APPROXIMATION METHODS**

Specifications: The Butterworth, Bessel and Chebyshev approximation methods can be designed into the circuit in Figure 2 by using a dual potentiometer and capacitive values of $C_1 = 0.015 \mu\text{F}$ , $C_2 = 0.0022 \mu\text{F}$ . The adjustable cutoff frequency range of these filters is 1,000 Hz to 10 kHz.					
Cutoff Frequency, Hz	Filter Approximation Method	Closest Digital Pot. $R_1$ Value, $\Omega$	Digital Pot. $R_1$ Code, decimal	Closest Digital Pot. $R_2$ Value, $\Omega$	Digital Pot. $R_2$ Code, decimal
1,000	Butterworth	8.203	21	94.141	241
	Bessel	5.078	13	93.359	239
	Chebyshev (3 dB Ripple)	3.516	9	33.984	87
2,000	Butterworth	3.906	10	47.266	121
	Bessel	2.344	6	46.484	119
	Chebyshev (3 dB Ripple)	15.625	40	17.188	44
3,000	Butterworth	2.734	7	31.250	80
	Bessel	1.563	4	31.250	80
	Chebyshev (3 dB Ripple)	10.547	27	11.328	29
10,000	Butterworth	0.781	2	9.375	24
	Bessel	0.391	1	9.375	24
	Chebyshev (3 dB Ripple)	3.125	8	3.516	9

## Combining Butterworth, Bessel and Chebyshev Second-Order Low-Pass Filters

All three approximation methods can be combined, with some limitations, in this circuit. Since there is a large variety of pole locations, the cutoff frequency range is 1:10. An example of a programmable filter with a cutoff frequency range of 1,000 Hz to 10 kHz is shown in Table 4.

## ERROR ANALYSIS OF PROGRAMMABLE FILTERS

### Absolute Accuracy of Circuit Elements

The nominal resistance of a 100 k $\Omega$  digital potentiometer (MCP42100), per data sheet specifications, varies approximately  $\pm 30\%$ . If the 10 k $\Omega$  digital potentiometer (MCP42010) is substituted for the MCP42100, the nominal resistance variance from part-to-part is specified at  $\pm 20\%$  for the MCP42010. When the 10 k $\Omega$  potentiometer is substituted, the capacitive values should be increased by 10X. For instance, in the Butterworth example of Table 1,  $C_1$  should be changed to 0.47  $\mu\text{F}$  and  $C_2$  changed to 0.18  $\mu\text{F}$ . When this is done, the codes to the potentiometer that can stay the same, remain unchanged. The change of the potentiometer from the MCP42100 (100 k $\Omega$ ) to the MCP42010 (10 k $\Omega$ ) will, in fact, decrease the values, as stated in Table 1, by 10X.

In this application circuit, it is suggested that the dual version of the digital potentiometer be used because there can be part-to-part variation of the nominal resistance ( $\pm 30\%$  for the MCP42100 and  $\pm 20\%$  for the MCP42010). With the dual potentiometer, resistor-to-resistor variation on chip is specified to a typical value of 0.2%. The resistance variation of these digital potentiometers is primarily dependent on the process variation of the sheet-resistance of a diffused p-silicon layer and the on-resistance of the internal switches.

If 20% accurate capacitors are used, the variability of this filter in a manufacturing environment is dominated by the capacitors.

### Wiper resistance

The wiper resistance of the MCP42100 digital potentiometer is approximately 125 $\Omega$  (typ) when  $V_{DD} = 5.5\text{V}$ . This wiper resistance appears as an error in the resistance value of the digital potentiometer only at lower programmed settings. For instance, with the MCP42100, the nominal resistance step for each code is equal to 100 k $\Omega$ /256, or 390.625 $\Omega$ . With a digital code setting of '1', the ideal nominal resistance is 390.625 $\Omega$ . However, with the added wiper resistance, this resistance is nominally 515.625 $\Omega$ .

## CONCLUSION

It is possible to design second-order, low-pass, programmable filters with one dual digital potentiometer, one amplifier and two capacitors.

## REFERENCES

- AN699, "Anti-Aliasing, Analog Filters for Data Acquisition Systems", Bonnie C. Baker, Microchip Technology Inc., DS00699, 1999.
- AN219, "Comparing Digital Potentiometers to Mechanical Potentiometers", Bonnie C. Baker, Microchip Technology Inc., DS00219, 2000.
- AN691, "Optimizing Digital Potentiometer Circuits to Reduce Absolute and Temperature Variations", Bonnie C. Baker, Microchip Technology Inc., DS00691, 2001.

---

**Note the following details of the code protection feature on Microchip devices:**

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

**Trademarks**

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELoQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


AmpLab, FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL, SmartShunt and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Application Maestro, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICkit, PICDEM, PICDEM.net, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, rLAB, rPIC, Select Mode, SmartSensor, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2004, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

**QUALITY MANAGEMENT SYSTEM  
CERTIFIED BY DNV  
== ISO/TS 16949:2002 ==**

*Microchip received ISO/TS-16949:2002 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona and Mountain View, California in October 2003. The Company's quality system processes and procedures are for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.*



## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200  
Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Atlanta

3780 Mansell Road, Suite 130  
Alpharetta, GA 30022  
Tel: 770-640-0034  
Fax: 770-640-0307

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848  
Fax: 978-692-3821

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071  
Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423  
Fax: 972-818-2924

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250  
Fax: 248-538-2260

#### Kokomo

2767 S. Albright Road  
Kokomo, IN 46902  
Tel: 765-864-8360  
Fax: 765-864-8387

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888  
Fax: 949-263-1338

#### San Jose

1300 Terra Bella Avenue  
Mountain View, CA 94043  
Tel: 650-215-1444  
Fax: 650-961-0286

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699  
Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733  
Fax: 61-2-9868-6755

#### China - Beijing

Unit 706B  
Wan Tai Bei Hai Bldg.  
No. 6 Chaoyangmen Bei Str.  
Beijing, 100027, China  
Tel: 86-10-85282100  
Fax: 86-10-85282104

#### China - Chengdu

Rm. 2401-2402, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-86766200  
Fax: 86-28-86766599

#### China - Fuzhou

Unit 28F, World Trade Plaza  
No. 71 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7503506  
Fax: 86-591-7503521

#### China - Hong Kong SAR

Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200  
Fax: 852-2401-3431

#### China - Shanghai

Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700  
Fax: 86-21-6275-5060

#### China - Shenzhen

Rm. 1812, 18/F, Building A, United Plaza  
No. 5022 Binhe Road, Futian District  
Shenzhen 518033, China  
Tel: 86-755-82901380  
Fax: 86-755-8295-1393

#### China - Shunde

Room 401, Hongjian Building, No. 2  
Fengxiangnan Road, Ronggui Town, Shunde  
District, Foshan City, Guangdong 528303, China  
Tel: 86-757-28395507 Fax: 86-757-28395571

#### China - Qingdao

Rm. B505A, Fullhope Plaza,  
No. 12 Hong Kong Central Rd.  
Qingdao 266071, China  
Tel: 86-532-5027355 Fax: 86-532-5027205

#### India

Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaughnessy Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

#### Japan

Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471-6166 Fax: 81-45-471-6122

#### Korea

168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5932 or  
82-2-558-5934

#### Singapore

200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-6334-8870 Fax: 65-6334-8850

#### Taiwan

Kaohsiung Branch  
30F - 1 No. 8  
Min Chuan 2nd Road  
Kaohsiung 806, Taiwan  
Tel: 886-7-536-4818  
Fax: 886-7-536-4803

#### Taiwan

Taiwan Branch  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Austria

Durisolstrasse 2  
A-4600 Wels  
Austria  
Tel: 43-7242-2244-399  
Fax: 43-7242-2244-393

#### Denmark

Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45-4420-9895 Fax: 45-4420-9910

#### France

Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - 1er Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20  
Fax: 33-1-69-30-90-79

#### Germany

Steinheilstrasse 10  
D-85737 Ismaning, Germany  
Tel: 49-89-627-144-0  
Fax: 49-89-627-144-44

#### Italy

Via Quasimodo, 12  
20025 Legnano (MI)  
Milan, Italy  
Tel: 39-0331-742611  
Fax: 39-0331-466781

#### Netherlands

P. A. De Biesbosch 14  
NL-5152 SC Drunen, Netherlands  
Tel: 31-416-690399  
Fax: 31-416-690340

#### United Kingdom

505 Eskdale Road  
Winnersh Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44-118-921-5869  
Fax: 44-118-921-5820